

**PHYSICS EXAM - ELECTRODYNAMICS**

Friday, January, the 12<sup>th</sup> - Duration: 1h

- No documents allowed. No calculator allowed.
- The marks will account for the **justifications**, the **critical analysis** of your results, as well as for the **writing** and the general **clarity** and **cleanness** of your documents.
- Every non homogeneous result presented without any comment will lead to a penalty on your final grade.

**Assignment I: Transient circuit ( $\approx 9$  pts)**

For the circuit depicted in Figure 1, the switch **opens** at  $t = 0$ . We know that the switch was closed from  $t = -\infty$ .

1. Determine the evolution in time of the intensity  $i_L(t)$  of the current through the coil and of the voltage across the coil  $v_L(t)$  as a function of the components ( $E$ ,  $L$ ,  $R_1$  and  $R_2$ ). Do not forget to justify all the steps.
2. Check that your expressions of  $i_L(t)$  and  $v_L(t)$  are consistent with the behavior of the circuit when  $t \rightarrow +\infty$ .
3. Compute the amount of energy denoted  $\Delta\varepsilon_L$  which has been stored in the coil from  $t = 0$  to  $t \rightarrow +\infty$ . What can you deduce from this expression about the behavior of the coil during this time interval?

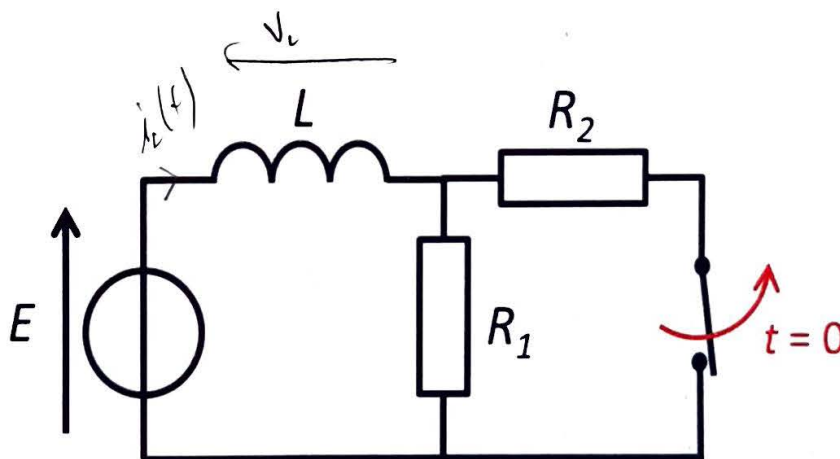


Figure 1

## Assignment 2: AC circuit ( $\approx 11$ pts)

We consider the circuit represented in Figure 2. It consists in an ideal voltage source of e.m.f.  $e(t) = E_m \cos(\omega t)$  on branch (SA) and two branches (SCA) and (SNA) composed of identical elements: two identical resistors of resistance  $R$  and two identical dipoles of complex impedance  $Z$ . The complex notation will be used throughout the whole assignment.

1. Express the current intensities in branches (SCA) and (SNA) and compare them.
2. Calculate the voltage differences  $V_C - V_A$  and  $V_N - V_A$ . Deduce the voltage difference  $\underline{u} = V_C - V_N$  between points C and N as a function of  $R$ ,  $Z$ , and  $\underline{e}$ .

Let's now consider that  $Z$  is an ideal capacitor of capacitance  $C_0$ .

3. Based on the behavior of the circuit at very low and very high frequencies, towards which limits does the voltage  $\underline{u}$  tend to at very low and very high frequencies?
4. Show that the transfer function can be written as in equation 1, and provide the expression of  $\omega_0$ . What is its dimension?

$$\underline{H}(j\omega) = \frac{\underline{u}}{\underline{e}} = \frac{1 - j \frac{\omega}{\omega_0}}{1 + j \frac{\omega}{\omega_0}} \quad (\text{equation 1})$$

5. Calculate the modulus  $G(\omega)$  and the phase  $\phi(\omega)$  of  $\underline{H}(j\omega)$ .
6. Represent schematically the evolution of  $\phi$  versus  $\omega$ . Indicate all characteristic quantities on your graph.
7. Explain why this circuit can be qualified as "phase shifter"?

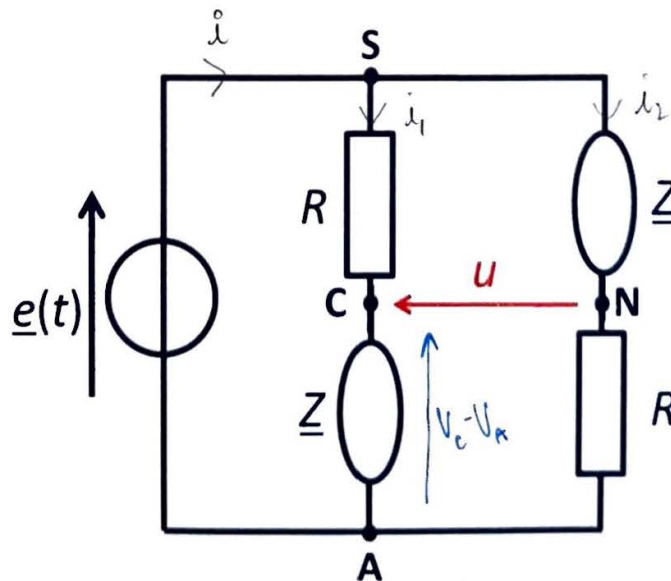


Figure 2