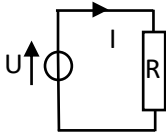


Exercise 1 : Ironing 8 pts +0.5pts bonus		
Elements of correction, expected items and grading scale		
<p><b>1- Meaning o the different physical quantities</b>            2000-2400W corresponds to the power used/received by the iron, noted P            dim (P) = dim(Energie)T<sup>-1</sup> and dim (Energie) = ML<sup>2</sup>T<sup>-2</sup> (kinetic energy for instance)            dim(P) = ML<sup>2</sup>T<sup>-3</sup>            220-240V corresponds to the voltage difference accros the iron noted U            dim (U) = dim(P)I<sup>-1</sup> (P= UI law with I the electric current intensity through the iron)            dim(U) = ML<sup>2</sup>T<sup>-3</sup> I<sup>-1</sup></p>	<p>0.5 pt for defining the quantities and their notation            0.5 pt for the dimension of P and U            0.5 pt for justifying the dimensions</p>	<p>/1.5</p>
<p><b>2- Physical and energy mechnisms at play</b>            The iron is made of a heating resistor (R). When plugged in, an electric current flows through the iron and energy is dissipated by Joule's effect.</p>  <p>An iron is a device that transforms <b>electric</b> energy into <b>thermal</b> energy</p>	<p>Expected words :            Resistor/resistance, Joule's effect, electric energy, thermal energy</p> <p><i>Bonus : 0.5 for a simplified eklectric scheme</i></p>	<p>/1   <i>Bonus /0.5</i></p>
<p><b>3- Electric current intensity</b>  <math>P = UI</math>            With the datasheet information:  <math>P = \frac{P_{max}+P_{min}}{2}</math> and <math>\Delta P = \frac{P_{max}-P_{min}}{2}</math>  <math>P = 2.2 \pm 0.2</math> kW  <math>U = \frac{U_{max}+U_{min}}{2}</math> and <math>\Delta U = \frac{U_{max}-U_{min}}{2}</math>  <math>U = 230 \pm 10</math> V  <math>I_{max} = \frac{P_{max}}{U_{min}} = \frac{2400}{220} = 10.909A</math>  <math>I_{min} = \frac{P_{min}}{U_{max}} = \frac{2000}{240} = 8.333A</math>  <math>I = \frac{I_{max} + I_{min}}{2} = 9.6212A</math>    <math>\Delta I = \frac{I_{max} - I_{min}}{2} = 1.2878A</math>  <math>I = 9.6 \pm 1.3</math> A            (give the points if correct result with differential method)</p> <p><math>R = U/I</math>  <math>R_{max} = U_{max}/I_{min} = 28.801152 \Omega</math>  <math>R_{min} = U_{min}/I_{max} = 20.1668 \Omega</math>  <math>DR = 4.31716 \Omega</math>  <math>R = 24.48399 \Omega</math>  <math>R = 24 \pm 5 \Omega</math></p>	<p>0.5 pt for literal expressions of P, ΔP, U, ΔU             0.5 pt for numerical values of P and U with their uncertainties.             0.5 pt for literal expressions of I<sub>max</sub>, I<sub>min</sub>, I and ΔI             0.5 pt for the result with correct formatting (digits and uncertainties)e             0.5 Ohm's law             0.5 final result (right unit, digits...)</p>	<p>/3</p>
<p><b>4- Consumed energy</b>            Consumed/received energy <math>E_c = P \cdot t</math> with t the duration of use  <u>Hypothesis</u>: no uncertainty on t or choose a realistic uncertainty, for instance <math>\Delta t = 1</math> min  <math>E_{c_{max}} = P_{max} \cdot t_{max}</math> and <math>E_{c_{min}} = P_{min} \cdot t_{min}</math>            If <math>\Delta t = 60s</math>  <math>E_{c_{max}} = 5184000J</math> and <math>E_{c_{min}} = 4080000J \Rightarrow E_c = 4,63 \pm 0,56</math> MJ            if <math>\Delta t = 0s</math>  <math>E_{c_{max}} = 5040000J</math> and <math>E_{c_{min}} = 4200000J \Rightarrow E_c = 4,62 \pm 0,42</math> MJ</p>	<p>0.5 literal expression of Ec            0.5 hypothesis on the uncertainty on t            0.5 numerical value of Ec with uncertainty , in proper format (accept a result with 1 significant digit)</p>	<p>/1.5</p>
<p><b>5- Cost for a 35 min use</b>            Price 0.10€/kWh (2020 cost...)  <math>= 0.1/(1000 \cdot 3600) \text{ €/J}</math>            Cost<sub>max</sub> = 0.144€            Cost<sub>max</sub> = 0.111€            Cost = 0.13 ± 0.02€</p>	<p>0.5 for unit conversion             0.5 for final result and uncertainty</p>	<p>/1</p>

<b>Exercise 2 : Diode</b>		/ 27+6
<p>1. Diode I-V curve in passive sign convention : see appendix for <math>u \leq e_S : I = 0</math> for <math>u \geq e_S : I = -\frac{e_S}{r_d} + \frac{U}{r_d} = (-0.3A) + (0.2\Omega^{-1}) \times U</math>.</p> <p>Plot : one can use <math>(U = 0, I = 0)</math>, <math>(U = e_S = 1.5V, I = 0)</math> and <math>(U = 1.75V, I = 5.10^{-2}A)</math> (accept other points, but -0.5 if 2 pts too close)</p> <p>Passive dipole, polarized, non linear (or piecewise linear)</p>		<p>0.5 convention 0.5 1 2 for plot with 3 well chosen points 1</p>
2.a. Circuit scheme with all information (see. end of correction)		1
<p>2.b. I-V curve of the generator : using two points with <math>U = E_g - R_g I</math> in Active sign convention : for instance <math>(U_1 = 1.25V, I_1 = 3.5.10^{-2}A)</math> and <math>(U_2 = 1.75V, I_2 = 2.5.10^{-2}A)</math>.</p> <p>Operating point : reading the intersection of the two curves <math>U_P = 1.60V + \frac{1.35cm}{18.8cm} \times 5.10^{-1}V</math> and <math>I_P = 2.10^{-2}A + \frac{1.55cm}{10.1cm} \times 5.10^{-2}A</math>. Hence <math>P(U_P = 1.636V, I_P = 2.77.10^{-2}A)</math> (accept any coherent value; significant digits decided after uncertainty calculation). Details about scale use expected, remove points otherwise</p>		<p>0.5 conv.+1 1.5 (with two points clearly shown)  1+1</p>
Overall uncertainty (detailed redaction below) : $U = (1.636 \pm 0.009)V$ and $I = (2.8 \pm 0.2).10^{-2}A$		1 (formatting only)
<p>Error sources and associated uncertainties : For instance (accept other organization if plausible; bonus for other relevant sources)</p> <ul style="list-style-type: none"> <li>- matter and medium : negligible</li> <li>- “man” (operator) :</li> </ul> <p>care while doing the projections and plots (line thickness, points positioning) : uncertainty on the intersection estimated as <math>\pm 2</math> line widths.</p> <p>Perpendicularity of the axes projections : uncertainty estimated as <math>\pm 2</math> line widths</p> <ul style="list-style-type: none"> <li>- means and method : 2 possible ways for reading (U,I) on the axes.</li> </ul>		<p>0.5 1 1</p>
<p><b>either</b> direct reading with the axes graduation : half a graduation uncertainty</p> <p>so <math>(\Delta I = 0.25.10^{-2}A</math> and <math>\Delta U = 0.013V</math> - 2 significant digits max.</p> <p>Given the graduations (large zoom), this uncertainty accounts for all sources of uncertainties (including operator ones)</p>		<p>0.5 0.5+1(-0.5 if <math>\Delta U</math> with 3 digits bonus 1</p>
<p><b>or</b> reading using a 20cm ruler and using a scale : <b>in place of the 2.5+bonus1 above</b> :</p> <p>With the total error on the projected position of the operating point of <math>\pm 4</math> line widths : We estimate 1 line width <math>\approx 0.5mm</math> which gives, using the intensity and voltage scales :</p> <p>4 line widths <math>\approx 4 \frac{0.5mm}{18.8cm} 0.5V \leq 6.10^{-3}V</math>,</p> <p>and 4 line widths <math>\approx 4 \frac{0.5mm}{10.1cm} 5.10^{-2}A \leq 10^{-3}A</math></p> <p>We must add the half a graduation uncertainty per reading, that is 1 graduation (= 1mm) per distance measured :</p> <ul style="list-style-type: none"> <li>for each reading on the axis</li> <li>for the scale measure of each axis</li> </ul>		<p>0.5 1  0.5 bonus 0.5</p>

<p>We get the operating point as (accept any coherent value) :</p> $U_{P,max} = 1.60V + \frac{1.45cm}{18.7cm} \times 0.5V + 6.10^{-3}V = 1.645V \text{ (literal relation no required)}$ $U_{P,min} = 1.60V + \frac{1.25cm}{18.9cm} \times 0.5V - 6.10^{-3}V = 1.627V$ <p>We get <math>\Delta U = \frac{U_{max} - U_{min}}{2} = 9.10^{-3}V</math></p> $I_{P,max} = 2.10^{-2}A + \frac{1.65cm}{10.0cm} \times 5.10^{-2}A + 10^{-3}A = 2.925.10^{-2}A$ $I_{P,min} = 2.10^{-2}A + \frac{1.45cm}{10.2cm} \times 5.10^{-2}A - 10^{-3}A = 2,611.10^{-2}A$ <p>and <math>\Delta I = \frac{I_{max} - I_{min}}{2} = 0.16.10^{-2}A</math></p> <p>Comment : The uncertainty due to the reading with a scale is 2 times smaller than with the line width</p>	<p>bonus 1</p> <p>bonus 0.5</p> <p>bonus 0.5</p> <p>bonus 1</p> <p>bonus 0.5</p> <p>bonus 0.5</p> <p>already graded</p> <p>bonus 0.5</p>
<p>2.c. Kirchhoff's voltage law</p> $\Rightarrow I = \frac{E_g - e_s}{r_d + R_g} \text{ and } U = e_s + (E - e_s) \frac{r_d}{r_d + R_g} = \frac{e_s R_g + E r_d}{r_d + R_g}.$ <p>Numerical application : <math>U = 1.636V</math> and <math>I = 2.7.10^{-2}A</math>. Remark : quantities <math>E</math>, <math>e_s</math>, <math>R_g</math> and <math>r_d</math> are known without uncertainty, so the number of significant digits is not defined.</p> <p>The values computed are in the uncertainty range obtained by graphical method.</p>	<p>1</p> <p>2</p> <p>0.5+0.5+ bonus</p> <p>0.5 comment on digits</p> <p>0.5</p>
<p>3.</p> <p>Using the I-V curve of the diode, we get <math>U(I = 10mA) = U_d = 1.55V</math></p> <p>Same uncertainty sources – accept results consistent with the previous question :</p> <p>half-graduation <math>\Delta U = 0.013V</math></p> <p>or <math>\pm 4</math> line widths <math>\approx \Delta U \leq 0.01V</math></p> <p>hence <math>U_d = 1.55 \pm 0.02V</math> or <math>\pm 0.01V</math> respectively (keeping only one digit for <math>\Delta U_d</math> for instance)</p>	<p>0.5</p> <p>0.5</p> <p>0.5 oonly format</p>
<p>4. <math>E_g - U_d = (R_p + R_g)I_d \Leftrightarrow R_p = \frac{E_g - U_d}{I_d} - R_g</math></p>	<p>2</p>
$R_{p,max} = \frac{E_g - U_{d,min}}{I_d} - R_g$ $R_{p,min} = \frac{E_g - U_{d,max}}{I_d} - R_g$ $\Delta R_p = \frac{1}{2} \frac{U_{d,max} - U_{d,min}}{I_d} = \frac{\Delta U_d}{I_d} = \frac{0.01V}{10mA} = 1.\Omega$ <p>and finally <math>R_p = (95 \pm 1)\Omega</math></p>	<p>1</p> <p>1 Num</p> <p>App+bonus0.5</p> <p>literal expression with <math>\Delta U_d</math></p> <p>0.5 only format</p>
<p>Remark : knowing all elements without uncertainty, we could deduce <math>R_p</math> directly :</p> $R_p = \frac{E_g - e_s}{I_d} - r_d - R_g.$ <p>Does not follow the question (with “Deduce”) and does not provide an uncertainty : give points on <math>R_p</math> only</p>	



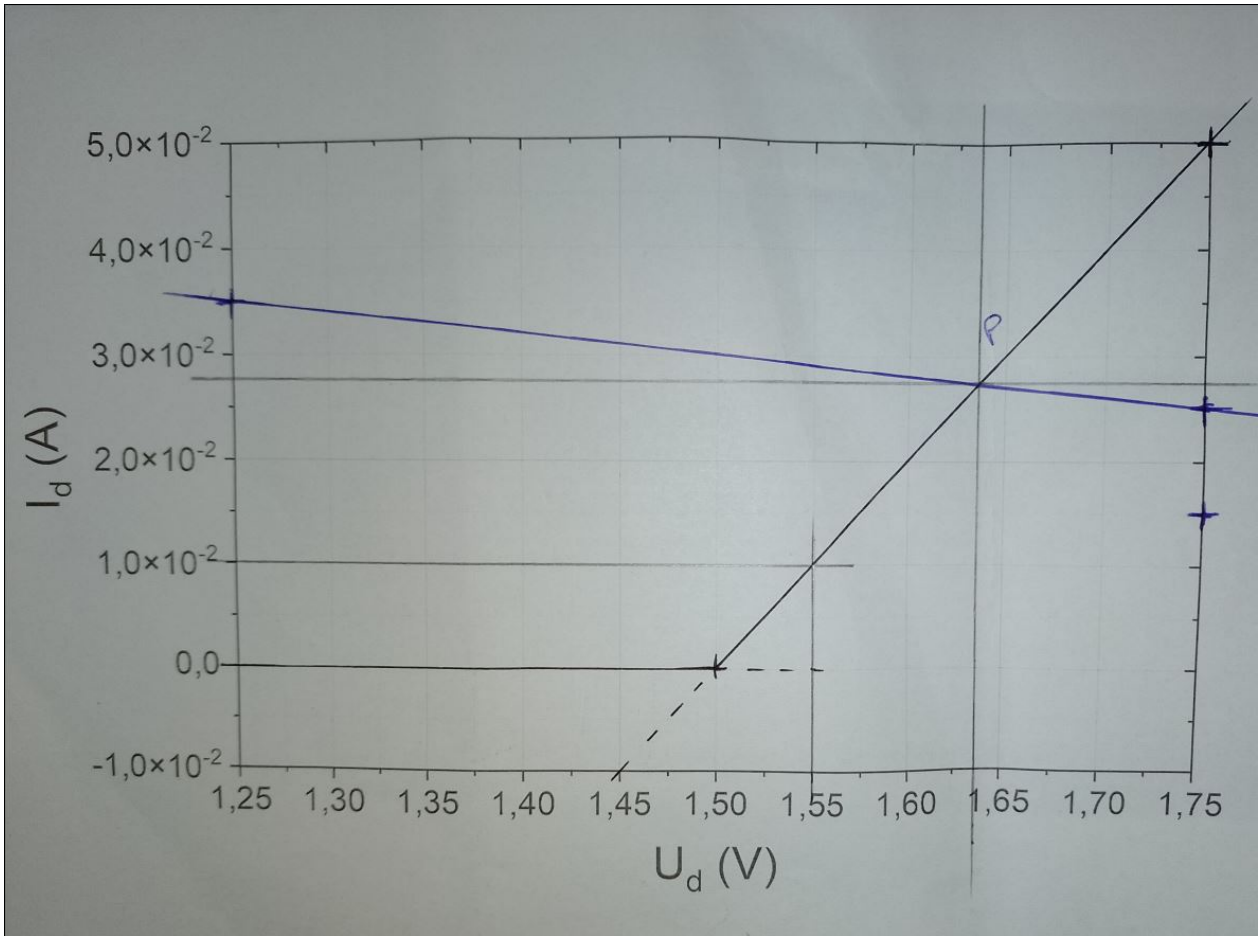


FIGURE 1 – Appendix 1

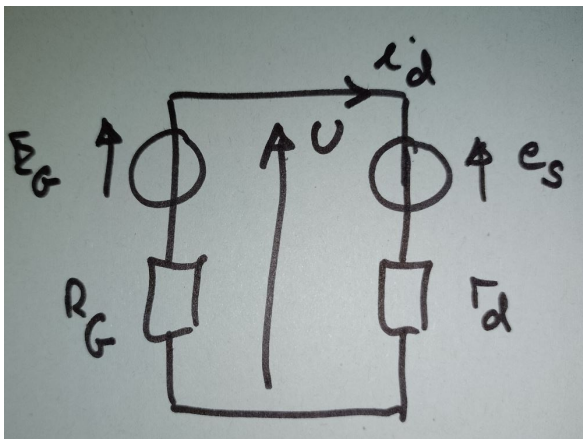

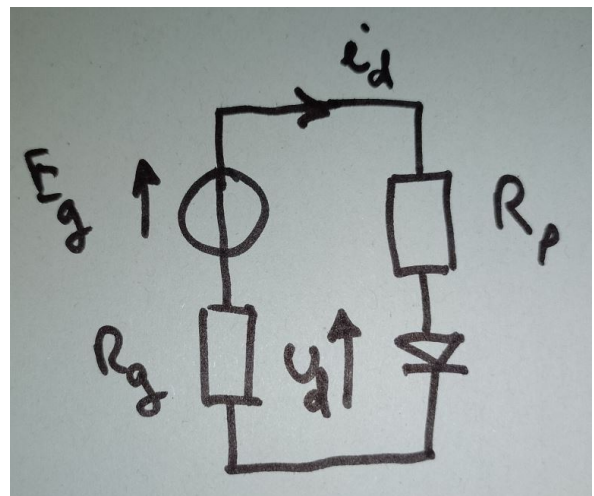(a) Equivalent circuit for questions 1 and 2



(b) Equivalent circuit for questions 3 and 4